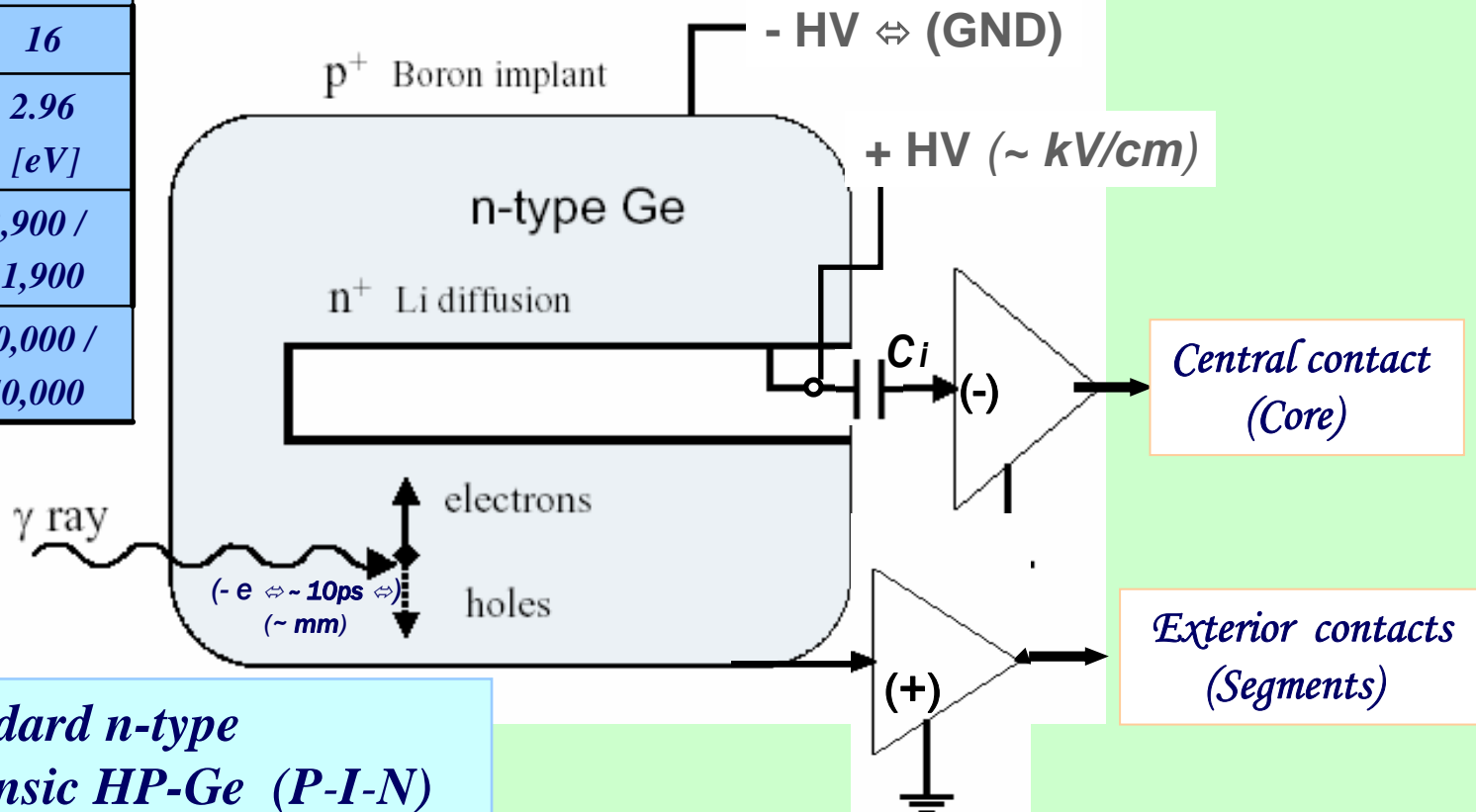


- ***Charge Sensitive Preamplifiers (CSP)
for the MINIBALL Array of Detectors***

- ***Core & Segments CSPs for 6-fold and 12-fold segmented and encapsulated detectors;***
- ***Principle of operation, schematics, PCBs;***
- ***Adjustments, troubleshooting, maintenance.***

A typical structure of a symmetric HP-Ge Detector

Parameter	Ge
Dielectric	16
Electron-hole pair E	2.96 [eV]
Mobility $e / \text{hole}(+)$	3,900 / 1,900
$e / \text{hole}(+)$ [cm ² /Vs]	40,000 / 50,000



- Standard n-type
- Intrinsic HP-Ge (P-I-N)
- Closed end
- Co-axial structure
- $I(o) \sim < 10$ [pA]

- $C_{det} \sim 35$ pF
- Collection time $\sim 100 - 1000$ ns


Semiconductors Detectors HP-Ge

<i>Parameter</i>	<i>Ge</i>	
<i>Dielectric constant</i> ϵ_0	16	$e(-) \Leftrightarrow 38,500$ [100]/[111]
<i>Electron-hole pair E</i> E_n [eV]	2.96 [eV]	$Hole(+)\Leftrightarrow 61,500$ [100]/[111]
<i>Mobility</i> <i>e / hole(+)</i>	3,900 / 1,900	@ [~ 300 ^o K]
<i>e / hole(+)</i> [cm ² /Vs]	40,000 / > 50,000	@ [~ 80 ^o K]

Analog Nuclear Electronics

- *Detector Signal collection*
- *Electronic Signal Processing*
- *Front-End : Preamplifier & Shaper*
- *Considerations on Detector Signal Processing*

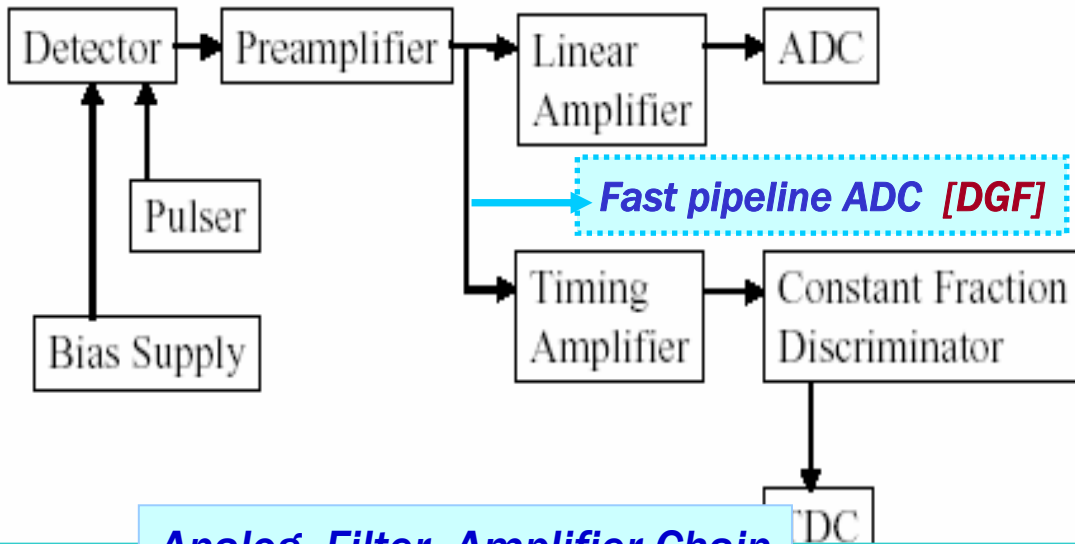
- **Specific issues about signal processing in gamma spectroscopy:**
 - a) **pulses** (delta, step, ~ Gaussian form)
 - b) they are **statistically distributed (BLR)**
- **Time \leftrightarrow frequency domain signal, circuit representation,**
- **A typical analog “front-end” electronics, namely a detector and charge sensitive preamplifier assembly**




[HP-Ge+CSP] + an **Analog** or **Digital Nuclear Electronics Spectroscopic Chain** is used in order to extract the:

\mathcal{E} , t ,

Analog Filter Amplifier Chain

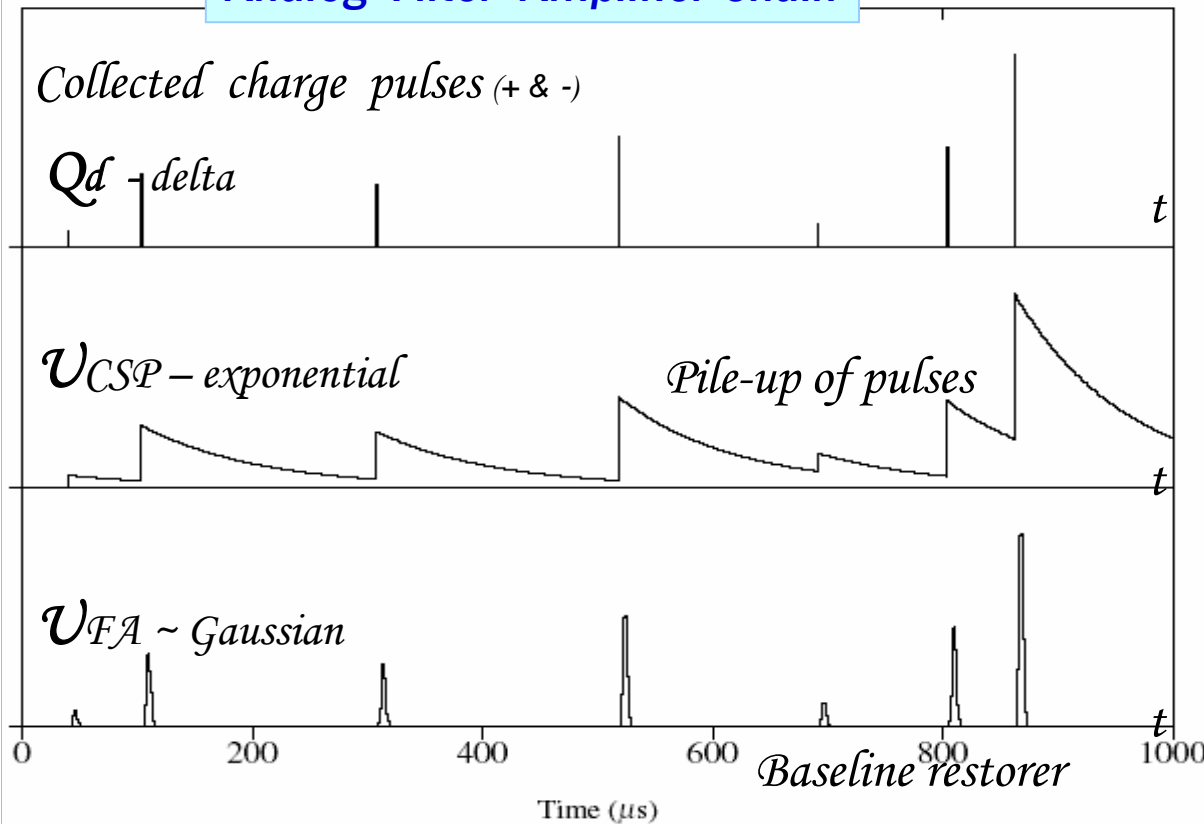


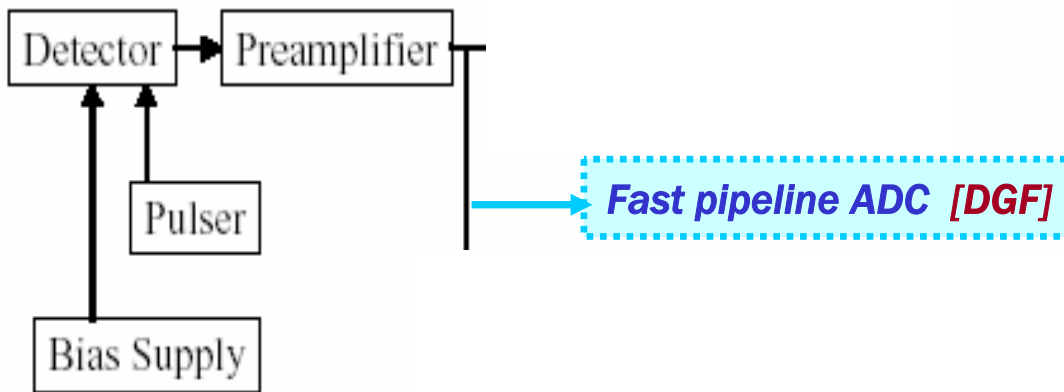


[HP-Ge+CSP] + an **Analog** or **Digital Nuclear Electronics Spectroscopic Chain** is used in order to extract the:

\mathcal{E} , t , *position (r, azimuth)*

Analog Filter Amplifier Chain

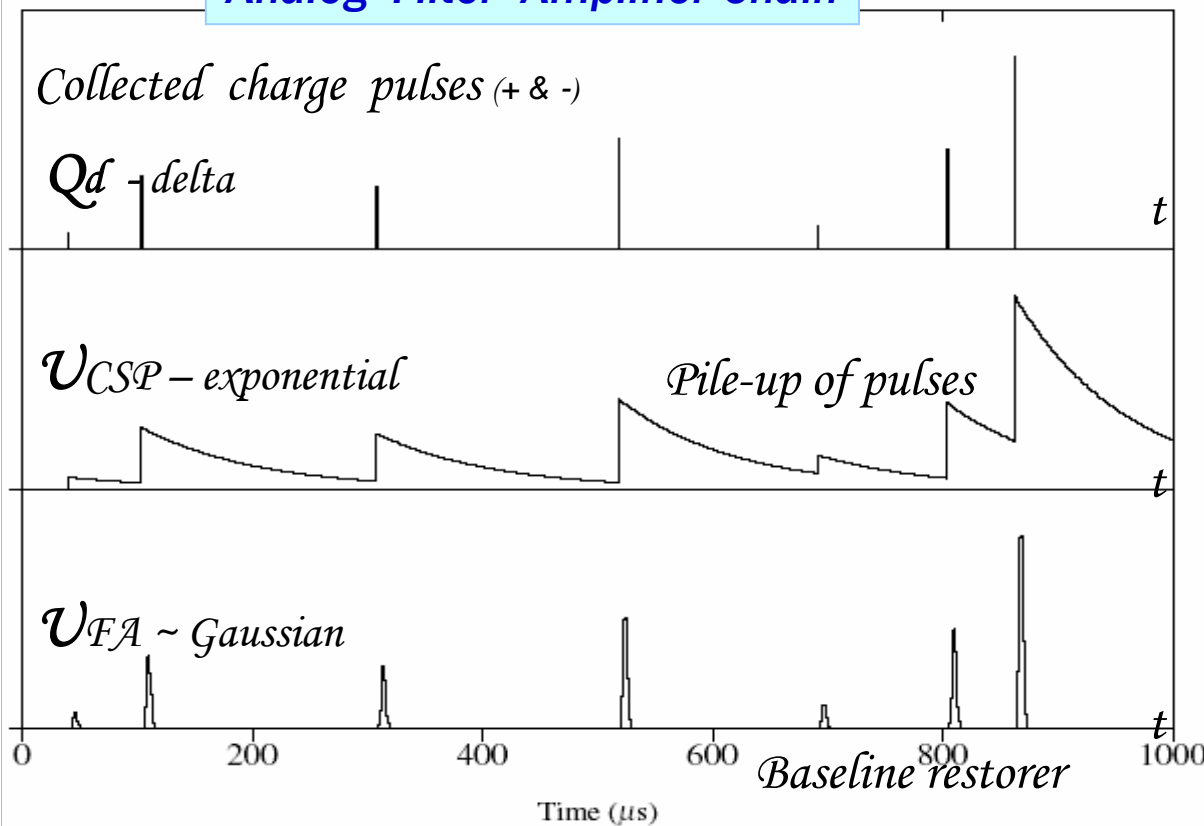


Fast pipeline ADC & [DGF]

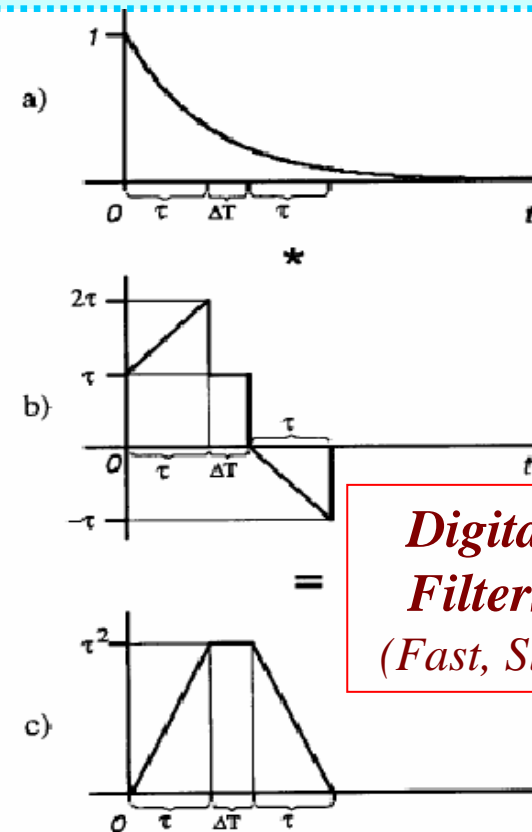

Digital Filters
(Fast, Slow)

Detector Signal Collection

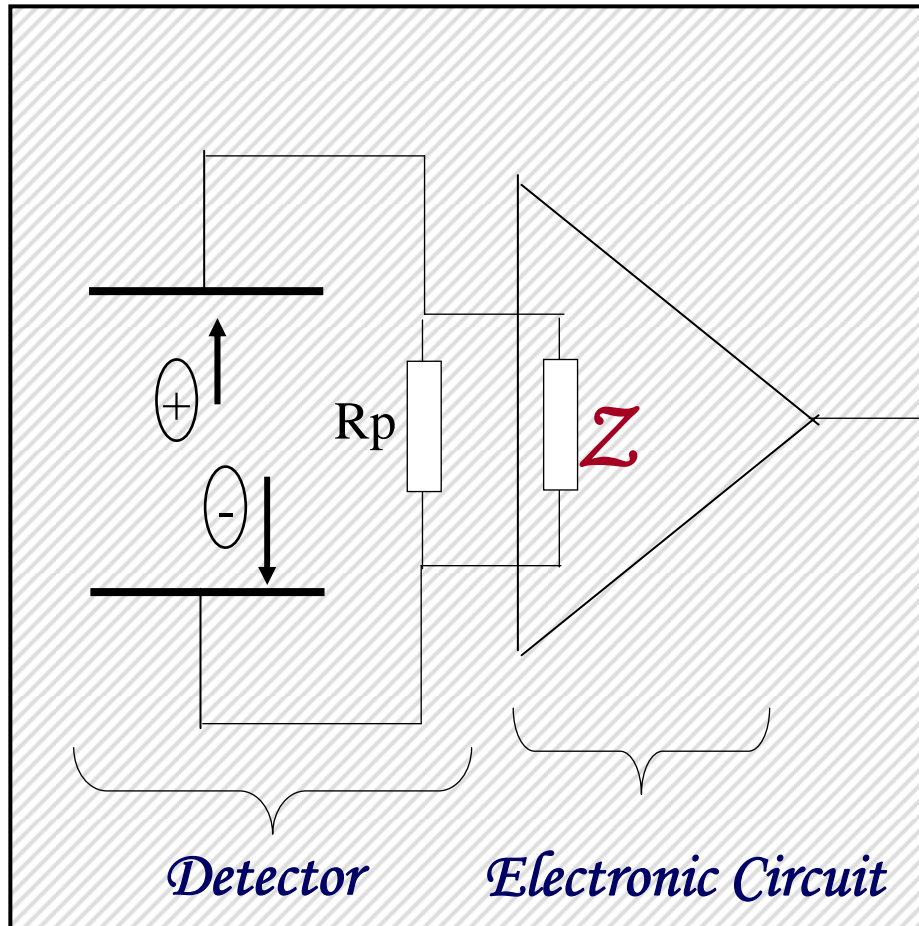


- a gamma ray crossing the Ge detector generates electron-hole pairs
- charges are collected on electrode plates (as a capacitor) \Leftrightarrow building up a voltage or a current pulse

Final objectives:

- amplitude measurement (E)
- time measurement (t)
- position (radius, azimuth)

Detector Signal Collection

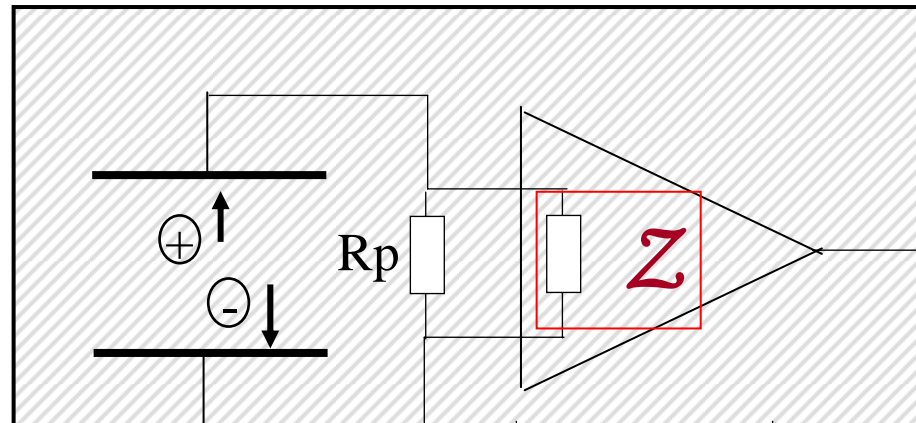

if Z is high,

- *charge is kept on capacitor nodes and a voltage builds up (until capacitor is discharged)*

- **Advantages:**

- *excellent energy resolution*
- *friendly pulse shape analysis \Leftrightarrow position*

- **Disadvantages:**

- *channel-to-channel crosstalk*
- *pile up above 40 k c.p.s.*
- *larger sensitivity to EMI*

if Z is low,

- *charge flows as a current through the impedance in a short time.*

- **Advantages:**

- *limited signal pile up (easy BLR)*
- *limited channel-to-channel crosstalk*
- *low sensitivity to EMI*
- *good time resolution*


- **Disadvantages:**

- *signal / noise ratio to low \Leftrightarrow worse resolution*

Charge Sensitive Preamplifier

Active Integrator (“Charge Sensitive Preamplifier” - CSP)

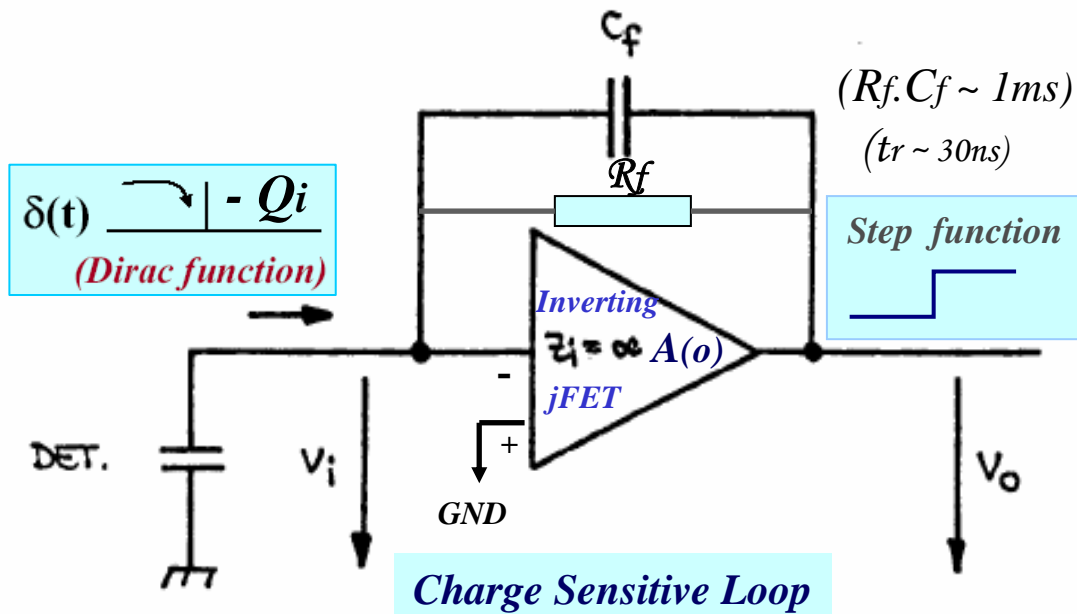- **Input impedance** very high (i.e. ~ no signal current flows into amplifier),
- **C_f/R_f** feedback capacitor /resistor between output and input,
- very large equivalent **dynamic capacitance**,
- **sensitivity** $A(q) \sim - Q_i / C_f$,
- **large open loop gain** $A_o \sim 15,000 - 150,000$
- **clean transfer function** (no ringing, no over shoots, no under shoots)





$C_i \sim$ “dynamic” input capacitance

$$C_i = \frac{Q_i}{v_i} = C_f (A + 1)$$


$$\Leftrightarrow C_i \sim 10 - 20,000 \text{ pF}$$

$$A_Q = \frac{dV_o}{dQ_i} \approx \frac{1}{C_f}$$

Pole - Zero cancellation technique

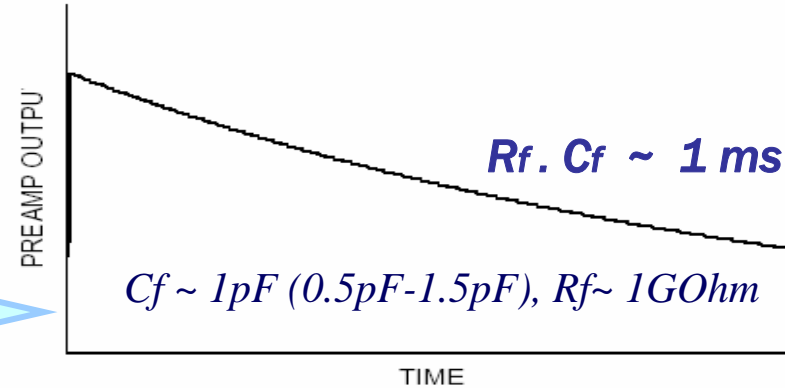
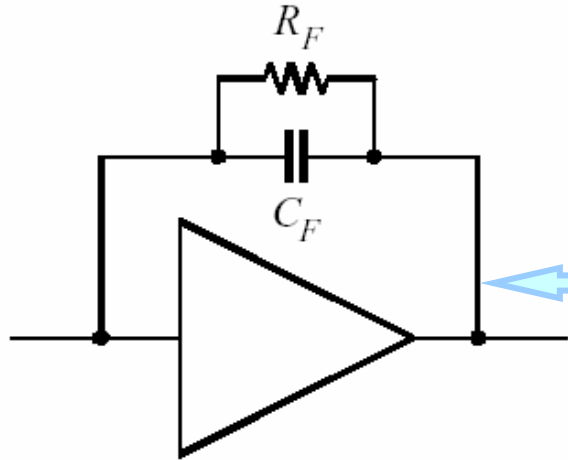


Add R_{pz} to differentiator:

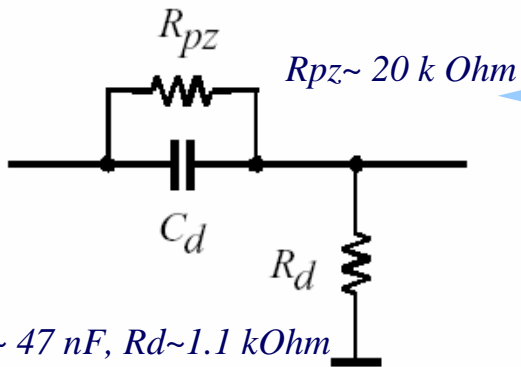

$C_d \sim 47 \text{ nF}$, $R_d \sim 1.1 \text{ k}\Omega$

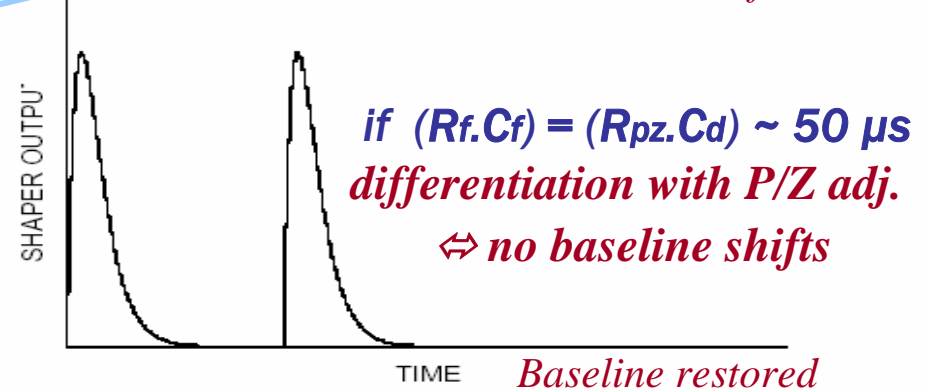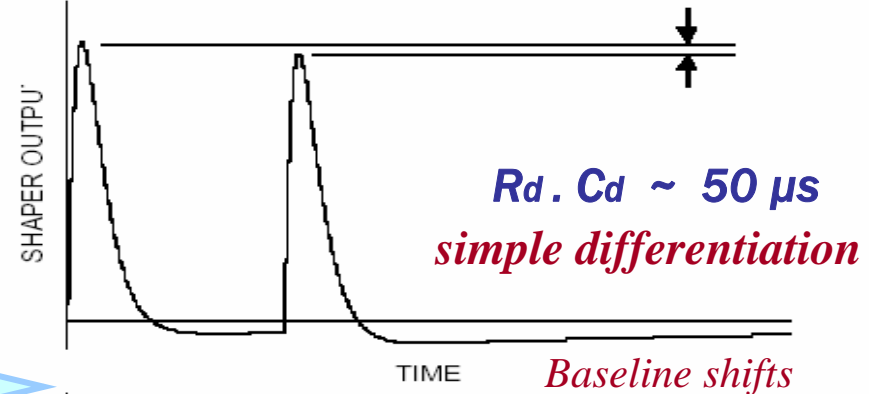“zero” cancels “pole” of preamp when $R_F C_F = R_{pz} C_d$




Parameter	IKP-Cologne (Miniball - jFET IF1320)
Sensitivity (mV / MeV)	~ 175 mV/MeV (single ended)
Resolution (Cd= 0pF; cold FET)	~ 600 eV
Slope (+ eV/ pF) [Cd]	< 10 eV / pF (cold FET)
Rise time (Cd= 0pF);	~ 15 ns (cold FET)
Slope (+ ns/ pF) [Cd]	~ 0.3 ns (~ 25 ns / 33 pF)
U(out) @ [50 Ohm] / Power [mW]	~ 4.5V / ~ 450 mW (+/- 12V ⇔ Op.Amp.LM-6172)
Saturation of the 1st stage @	equiv. ~100 MeV (@ ~60mW_jFET)
Open Loop Gain	~ 20,000

MINIBALL

Charge Sensitive Preamplifier Specifications

- *By design optimized*
Transfer Function
- **Crosstalk requirements**
less than 10^{-3} core-segment

Noise Bandwidth VS. Signal Bandwidth

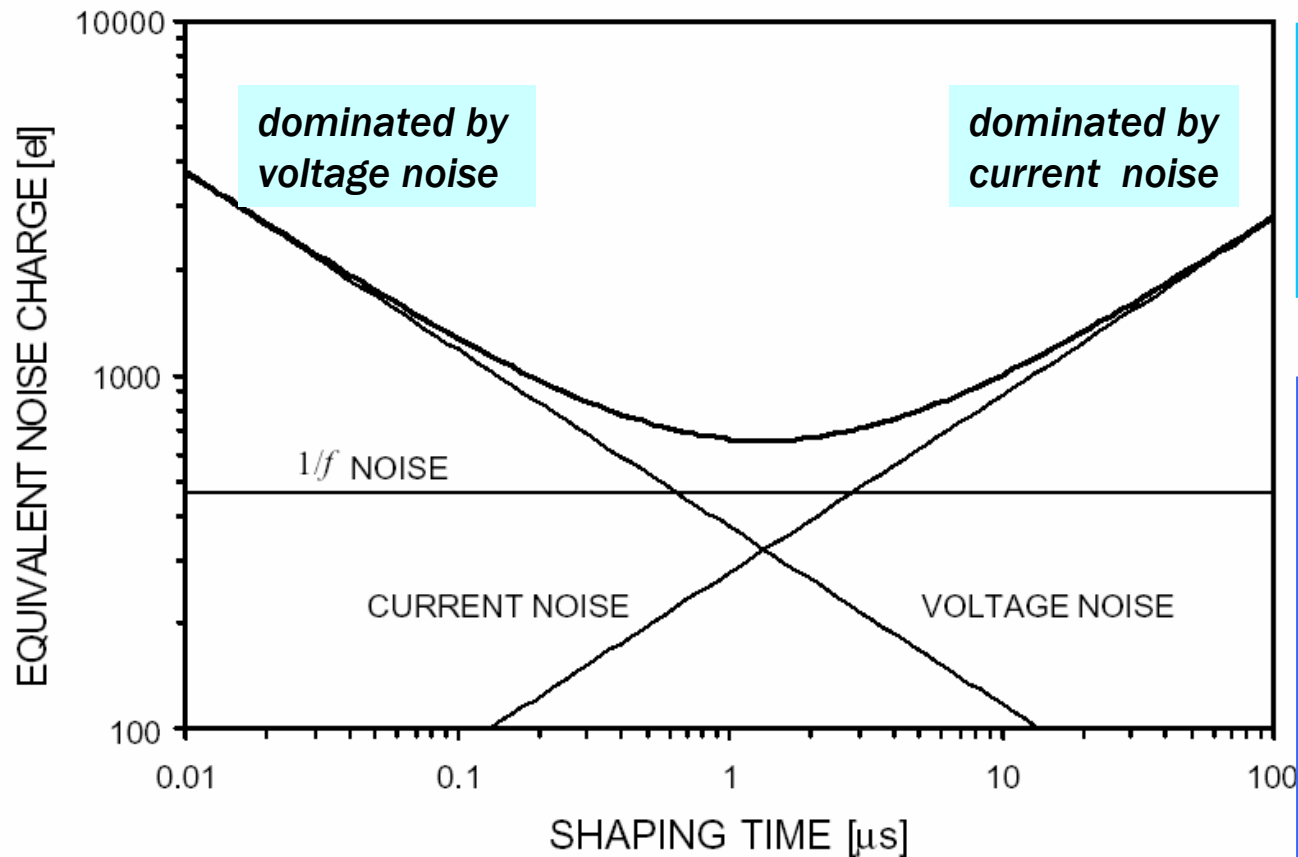

• the **equivalent noise charges Q_n** assumes a minimum when the **current and voltage contributions are equal**

- **current noise** $\sim (RC)^2$
- **voltage noise** $\sim 1/(RC)$
- **1/f noise** $\sim C_d$

$$Q_n^2 = \left(\frac{e^2}{8}\right) \left[\left(2q_e I_D + \frac{4kT}{R_P} + i_{na}^2 \right) \cdot \tau + \left(4kTR_S + e_{na}^2 \right) \cdot \frac{C_D^2}{\tau} + 4A_f C_D^2 \right]$$

$i_{np}^2 = \frac{4kT}{R_P}$

current noise $\propto \tau$

independent of C_D

voltage noise $\propto 1/\tau$

$\propto C_D^2$

1/f noise independent of τ


$\propto C_D^2$

$$e_{na}^2 = e_{nw}^2 + \frac{A_f}{f}$$

↑ ↑




"white noise" 1/f noise (can also originate in external components)

MINIBALL Charge Sensitive Preamplifier

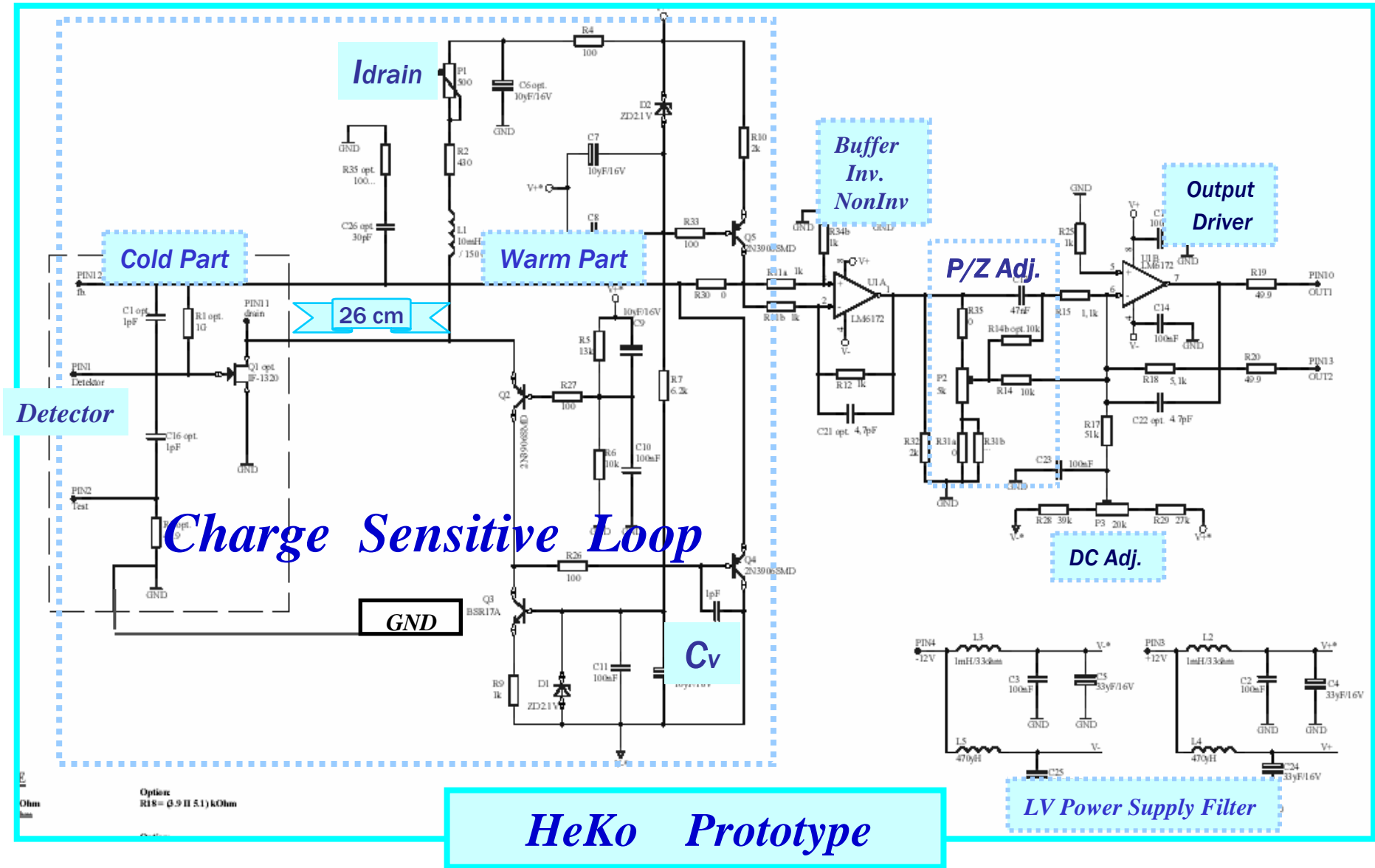

[HeKo] - Family of CSP

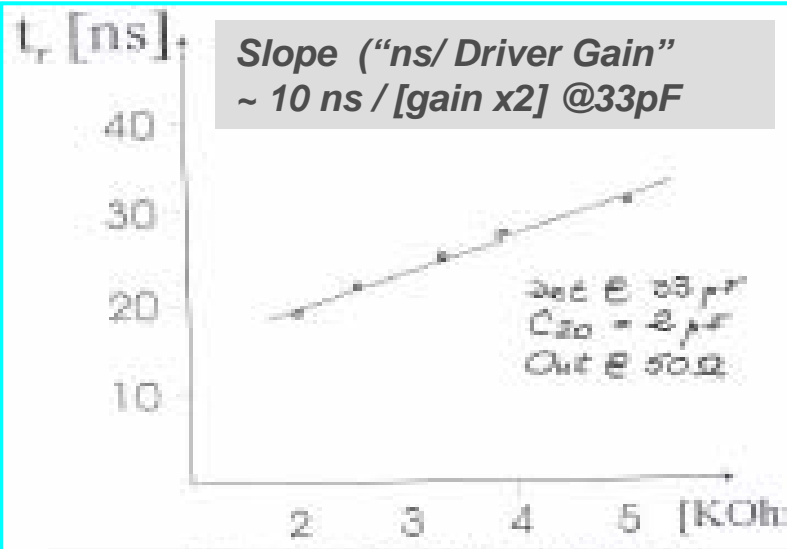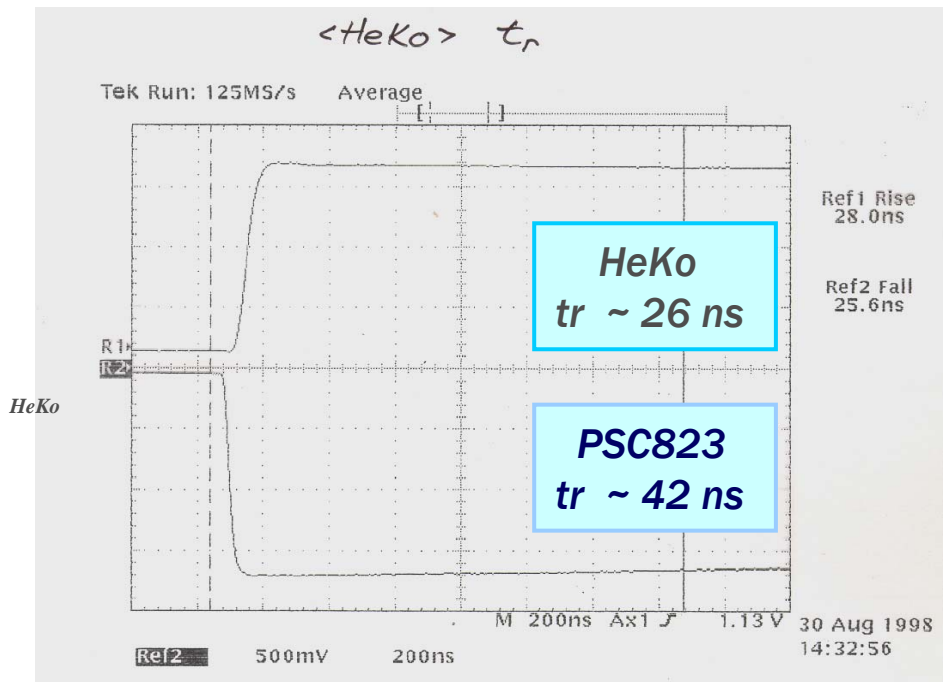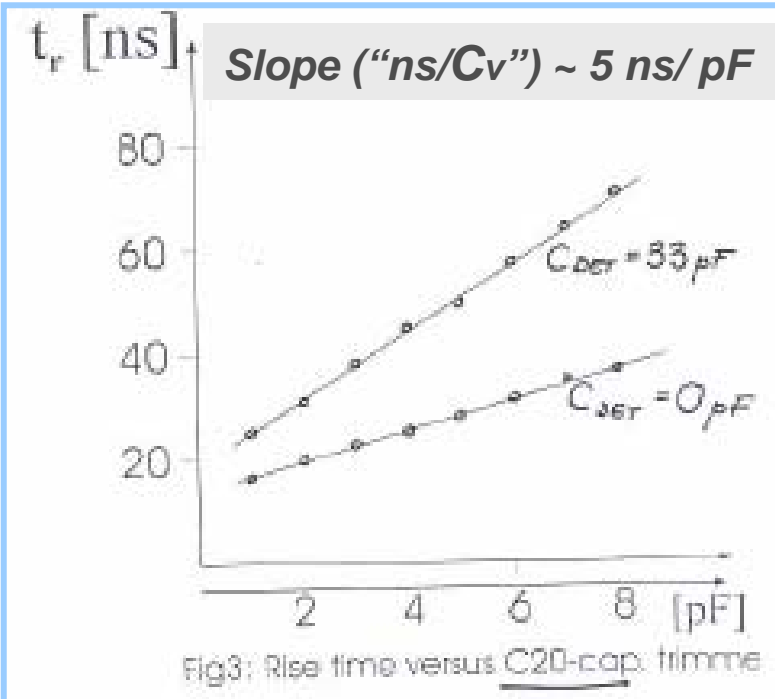consequences of various adjustments
gain, rise time, slope, ringing



[http://www.nsg.tsl.uu.se/agata/padova-sep2002/slides/Pascovici/Outlook_CSP\(2\).pdf](http://www.nsg.tsl.uu.se/agata/padova-sep2002/slides/Pascovici/Outlook_CSP(2).pdf)

Adjustments

Miniball warm CSP
type **HeKo**


~~NOT Connected~~

Rf & Cf JFET
Test In.


I Drain (JFET) (Step 1)

Cv - trimmer (bandwidth adj.)

S1 + S3 Inverting / Non_Inverting

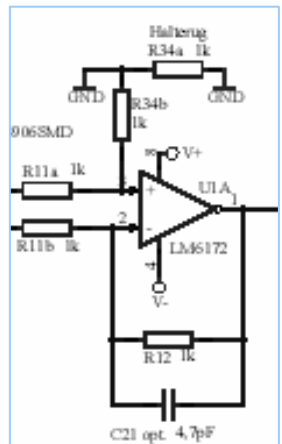

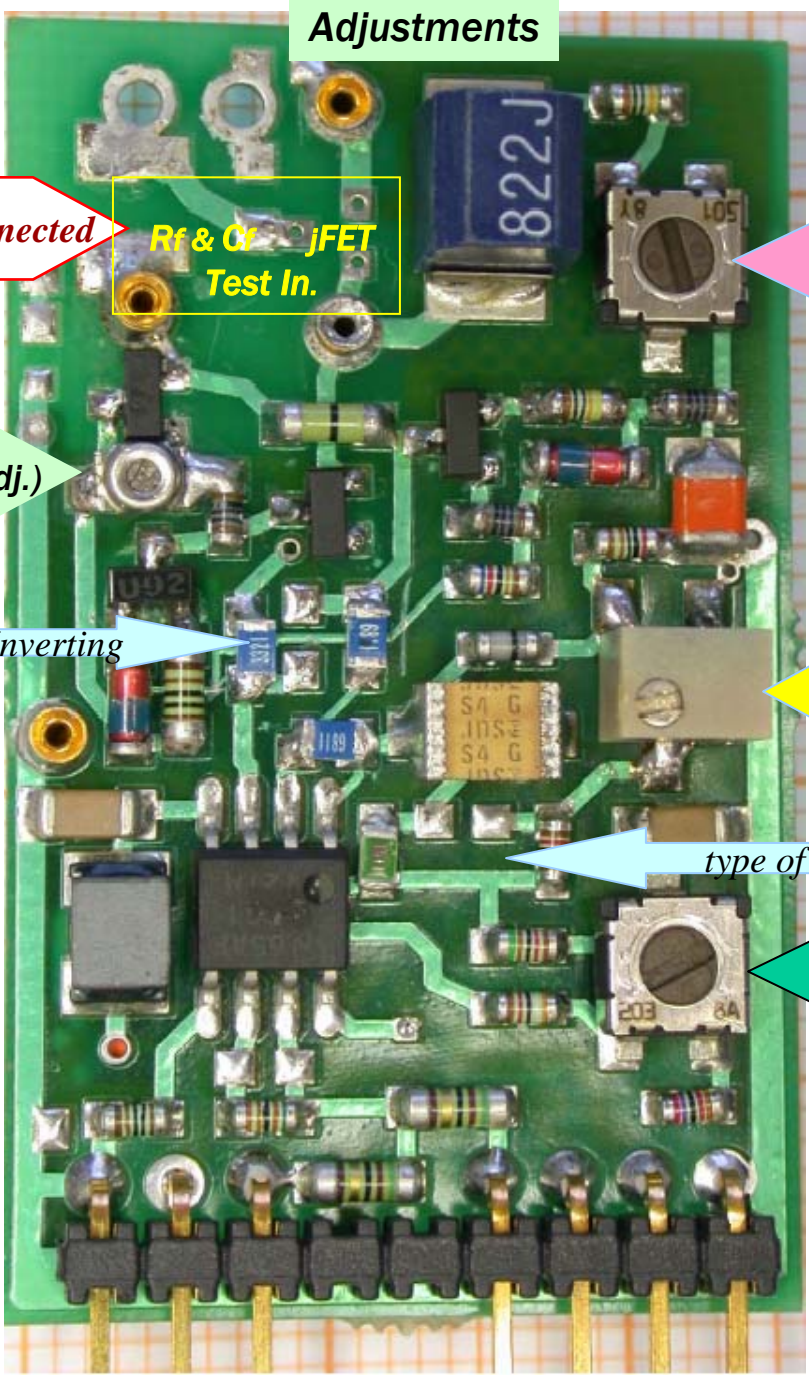
N.B. by default "Inverting"
(R11b and R34b - ON)




P/Z Adj. (Step 2)
(Helitrim. 11 turns)

type of P/Z cancellation S5

DC Level Adj. (Step 3)

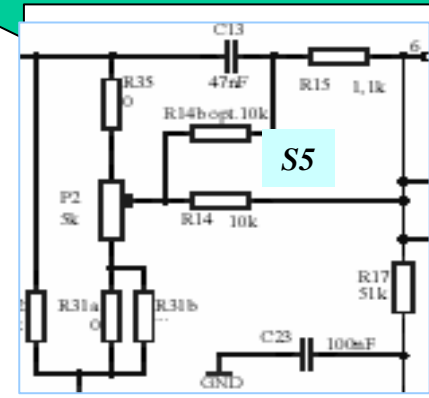


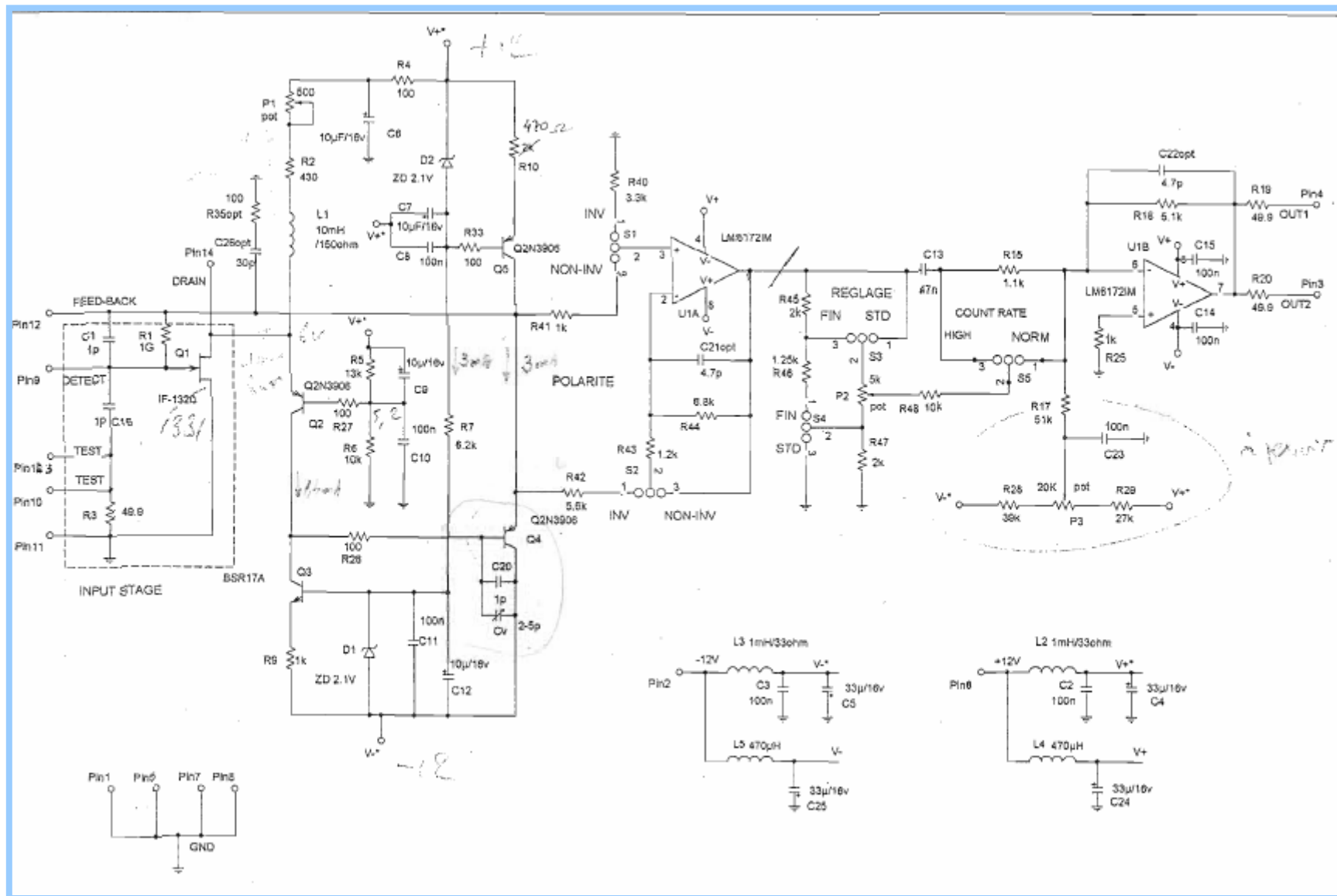

Adjustments

**Miniball warm CSP
type PSC 823**

~~NOT Connected~~

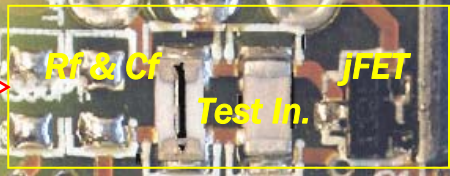

I Drain (JFET) (Step 1.)

S1 **Inverting / Non Inverting**


Inverting / Non Inverting S2

Cv - trimmer (bandwidth adj.)

P/Z Adj. (Step 2)



S3 **Range R(P/Z)
(if NO Helitrim.!)**



**Range R(P/Z) S4
(if NO Helitrim.!)**

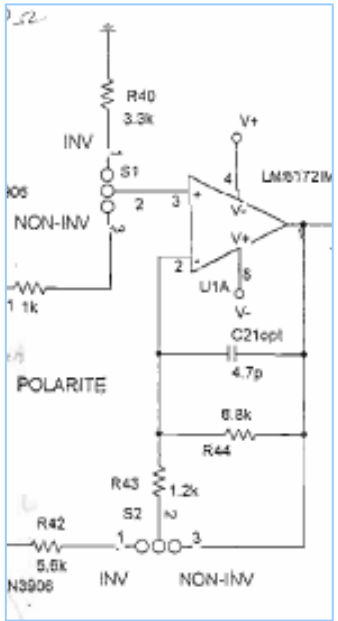


Count Rate High/Low S5

DC Level Adj. (Step 3)

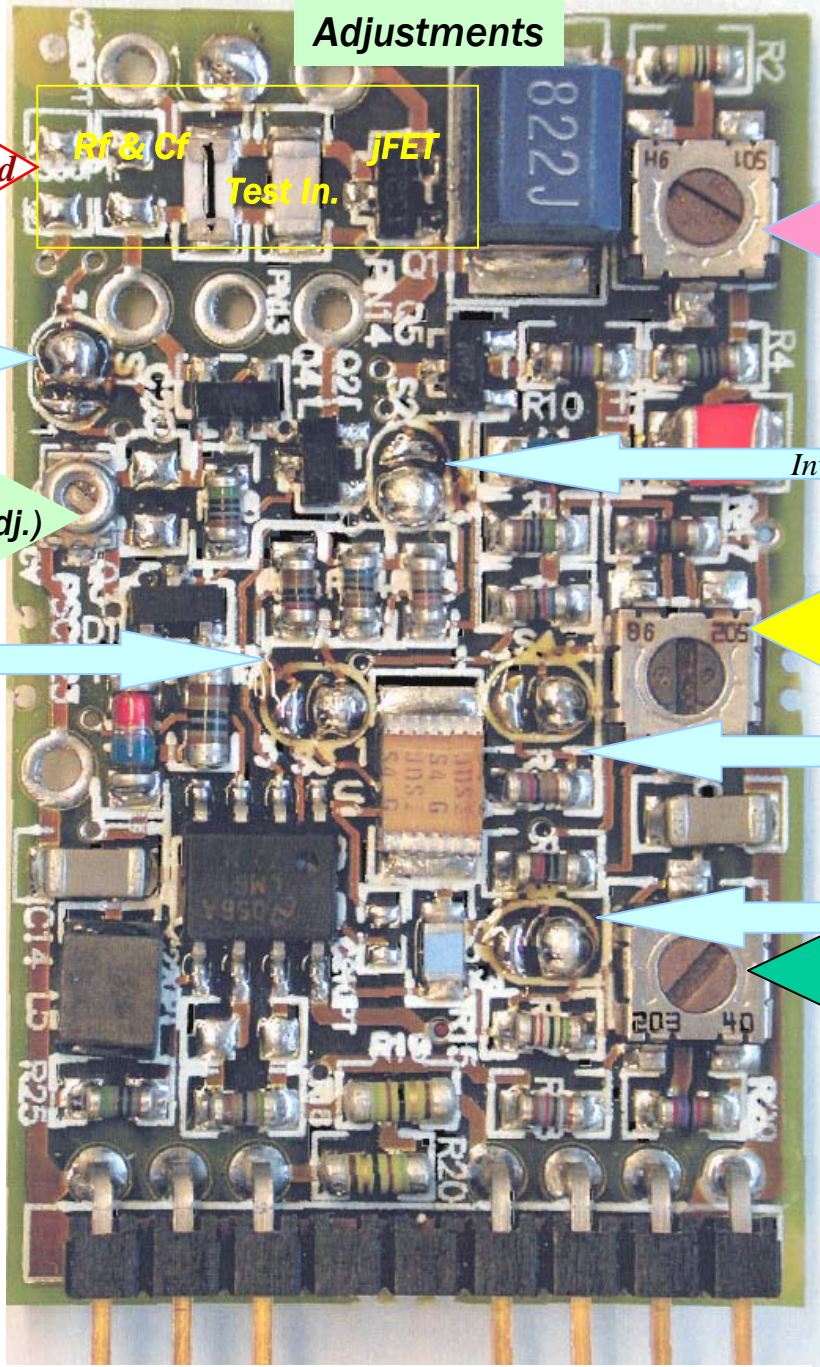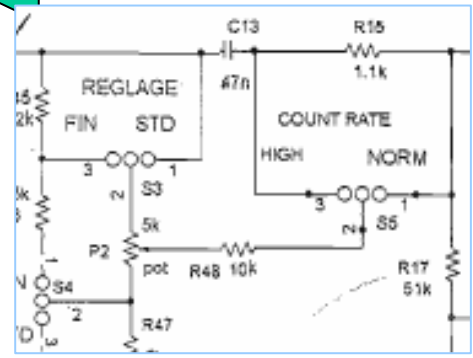

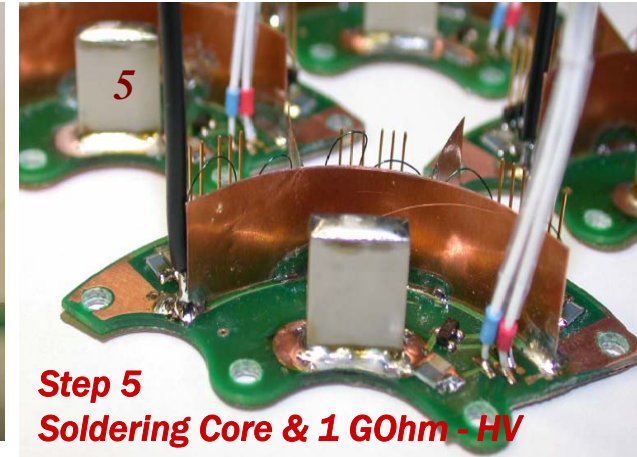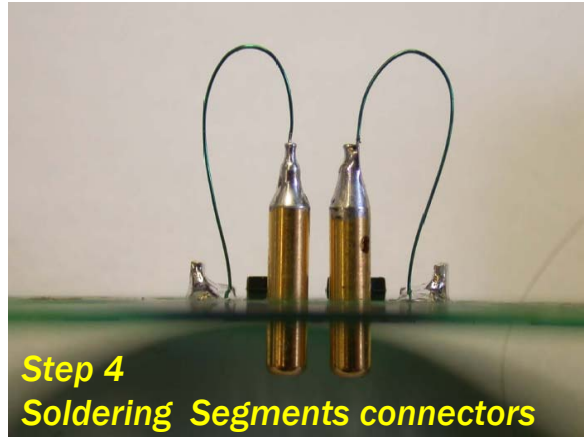

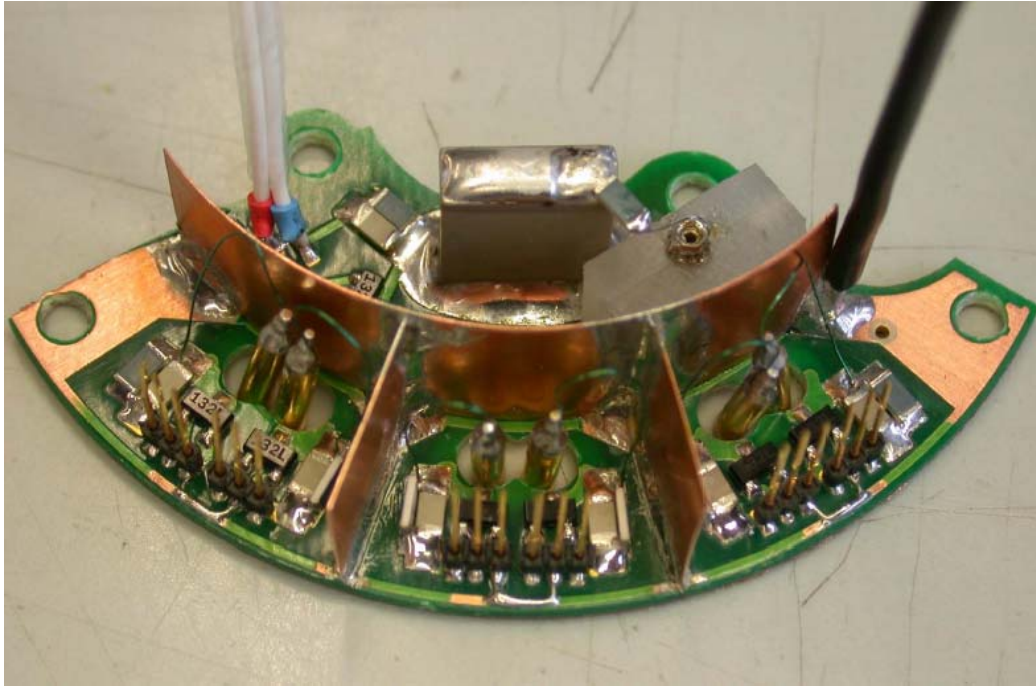Technological steps in building - mounting a set of cold parts of CSPs on a 6_fold segmented encapsulated Miniball Detector



*Miniball
cold preamplifier set*

*- new spare part (model)
reworked at IKP-Köln
(Jan. 2007)*



*... and some still working
cold parts but with:*

- bad segments shielding,*
- some cold solder joints,*
- almost braking wires*

Miniball Cryostat & warm motherboards



D1 & D3 Motherboards with CSPs clockwise rotated ⇔ OK!



some D2 Motherboards with CSPs counterwise rotated ⇔ Wrong!



- related problems

- PT 100 coaxial cable (x2)
- Metal bottom ring for BNCs